

Differential and Single-Ended ADC

# **Differential and Single-Ended ADC**

### Introduction

Author: Kristian Saxrud Bekken, Microchip Technology Inc.

A common requirement for microcontroller applications is the need to sense the real world in one way or another. This requires bridging the gap between the digital dimension of a microcontroller and the analog realm of the real world. In most cases, this is accomplished by using a sensor that translates the magnitude of a physical phenomenon to an analog voltage which is routed to a pin on the microcontroller. Lastly, a dedicated part of the microcontroller called an analog-to-digital converter, also referred to as an ADC or A/D converter, transforms the analog voltage to a digital value to be further processed by the microcontroller.

Most analog sensors either output their measured value as a single analog voltage signal or as a difference between two analog voltage signals. The two concepts are referred to as single-ended signaling and differential signaling, respectively.

This white paper provides a high-level introduction to A/D conversion of single-ended and differential analog signals by presenting the main advantages and drawbacks for the two approaches, as well as a selection of common applications and useful considerations.

## **Table of Contents**

Intro	Introduction1					
1.	Single-Ended Operation					
	1.1.	General Concept				
	1.2.	Advantages and Drawbacks				
	1.3.	Typical Applications				
2.	Differe	ntial Operation5				
	2.1.	General Concept				
	2.2.	Advantages and Drawbacks6				
	2.3.	Typical Applications				
3.	Considerations7					
4.	Revision History					
The Microchip Website						
Pro	Product Change Notification Service9					
Customer Support9						
Pro	Product Identification System10					
Mic	rochip I	Devices Code Protection Feature				
Leg	al Notio	ce				
Trac	Trademarks					
Quality Management System						
Woi	Worldwide Sales and Service					

### 1. Single-Ended Operation

#### 1.1 General Concept

The simplest and most widely used analog sensors provide single-ended signals. These are designed to be connected to the same ground level as the microcontroller and to provide their measurement result as an analog voltage signal on a single wire referenced to this common ground. All basic ADCs support single-ended operation.

An ADC can be designed to operate in different ways, and the amount of time required to perform an analog-to-digital conversion will vary between ADCs. Regardless, the result is a digital representation of the analog input value. The digital value will typically be an integer between 0 and  $2^{n}-1$ , where n is the resolution of the ADC in bits. An integer value of 0 means that the analog voltage level is the same as ground, while the maximum value  $(2^{n}-1)$  corresponds to the level of what is referred to as the ADC voltage reference  $(V_{ref})$ . The voltage reference defines the conversion range of the ADC, which for single-ended operation means that an analog input above this level still produces the maximum digital value, while an input below ground level gives a digital value of 0. In most cases, the ADC voltage reference can be selected among different levels between ground and the microcontroller supply voltage in order to utilize as much of the ADC resolution as possible for inputs in a given voltage range.

A 12-bit single-ended ADC will most likely have an output range of [0, 4095]. If the selected  $V_{ref}$  is 2.0V, and the analog input signal is 0.5V, the corresponding digital value can be calculated as follows:

#### Equation 1-1. Example - 12-bit Single-Ended Conversion

ADC Output = 
$$\left(\frac{\text{Input}}{V_{ref}}\right)$$
 · Total ADC Counts  
=  $\left(\frac{0.5V}{2.0V}\right)$  · 4096  
= 1024

### 1.2 Advantages and Drawbacks

Whether single-ended operation is the best choice in a given setting depends on the specific application. Below are some of the main advantages and drawbacks associated with this approach.

Main advantages:

- Both sensors and microcontrollers are available at very low cost
- · Occupies only one analog microcontroller input per sensor
- · In most cases conceptually simple and easy to use
- · Large selection of available sensors and microcontrollers

Main drawbacks:

- Sensitive to noise along the analog signal path
- Sensitive to common-mode noise on the ground and reference voltage levels of the microcontroller
- The signal path between the sensor and the microcontroller should be as short as possible to minimize noise and ground-level differences
- Conditioning circuitry that adds cost and unwanted dynamic effects might be needed

### 1.3 Typical Applications

There are numerous types of single-ended analog sensors available. Some of the most common use-cases in microcontroller applications are:

- Potentiometers for measuring angle or position
- Light intensity measurement
- Infrared and ultrasonic range measurement

• Gas and air quality measurement

### 2. Differential Operation

#### 2.1 General Concept

A differential ADC measures the voltage difference between two inputs. This can be essential in certain applications as some measurement concepts require two output signals instead of one to quantify the physical property of interest. Sensors that implement such concepts typically provide their output value as the voltage difference between two signals, also known as a differential signal. Other sensors might provide a differential output for added robustness even though the measurement itself generates a single-ended signal.

A basic single-ended ADC can be used to measure a differential signal by connecting each of the two inputs to a single-ended ADC channel, sampling them sequentially, and comparing the results in software. Other so-called pseudo-differential approaches also exist, but all have little effect on dynamic common-mode noise since the two inputs are sampled at different times. An ADC that supports differential operation would be the preferred option when using such sensors since the ADC will then be capable of directly converting the difference between the two varying voltage levels to a digital value.

When connecting a differential analog sensor to a microcontroller one of the signals in the differential pair is defined as the positive input while the other is defined as the negative input. By definition, the value of the differential signal is the voltage of the positive input referenced to the negative input. The positive and negative designation of each signal determines the polarity of the differential signal, defining it as positive when the positive input is larger than the negative input and negative if the negative input is larger than the positive input.

**Note:** A negative differential signal does not imply a negative voltage on any of the two corresponding inputs, as this would be outside the specifications of most microcontrollers. It only means that the negative input is larger than the positive input.

The voltages of each signal in a differential pair are in most cases referenced to the same ground level as the microcontroller, but in some applications, the ground level of the sensor could be isolated from that of the microcontroller.

Like single-ended operation, the ADC voltage reference  $(V_{ref})$  is often configurable and determines the range of input voltages that will be converted. But for differential operation, the input range is extended in the negative direction such that differential voltages of  $-V_{ref}$  and  $V_{ref}$  gives the minimum and maximum input values, respectively.

The corresponding digital values for the valid analog input range  $[-V_{ref}, V_{ref}]$  can be represented in different ways depending on the ADC. A common output is signed integers in the range  $[-2^{n-1}, 2^{n-1}-1]$ , where n is the resolution of the ADC in bits. The specific integer format can also vary, but 2's complement is widely used.

A 12-bit differential ADC with signed output will commonly give digital values in the range [-2048, 2047]. If  $v_{ref}$  is 2.0V and the analog differential signal is -0.5V, the corresponding digital value can be calculated as shown below. Notice how the total number of ADC counts is divided by 2 as the 4096 available ADC counts are distributed on each side of zero.

#### Equation 2-1. Example - 12-bit Differential Conversion with Signed Output

ADC Output = 
$$\left(\frac{\text{Differential Input}}{V_{ref}}\right) \cdot \left(\frac{\text{Total ADC Counts}}{2}\right)$$
  
=  $\left(\frac{-0.5V}{2.0V}\right) \cdot \frac{4096}{2}$   
=  $-512$ 

Another commonly used output format is direct binary mapping using unsigned integers in the range  $[0, 2^{n}-1]$ , where n is the ADC resolution in bits.

The unsigned output range of a typical differential 12-bit ADC will be [0,4095]. If  $v_{ref}$  is 2.0V and the analog differential signal is -0.5V, the corresponding digital value can be calculated as shown below. Notice how an offset of 2048 is added to make an input of 0.0V correspond to the center of the output range, and how the total number of ADC counts is divided by 2 as the 4096 available ADC counts are distributed on each side of zero before adding the offset.

© 2019 Microchip Technology Inc.

#### Equation 2-2. Example - 12-bit Differential Conversion with Unsigned Output

ADC Output = 
$$\left( \left( \frac{\text{Differential Output}}{V_{ref}} \right) \cdot \left( \frac{\text{Total ADC Counts}}{2} \right) \right) + \text{ADC Counts at Zero}$$
  
=  $\left( \left( \frac{-0.5V}{2.0V} \right) \cdot \frac{4096}{2} \right) + 2048$   
=  $(-512) + 2048$   
=  $1536$ 

#### 2.2 Advantages and Drawbacks

Differential analog-to-digital conversion is often selected for demanding environments that require higher performance and robustness compared to the more common single-ended approach. Below are some of the main advantages and drawbacks that could help decide whether differential operation is required for a specific application.

Main advantages:

- Rejects noise along the signal path if the positive and negative inputs are twisted or routed together since any noise then affects both signals equally
- Rejects common-mode noise on the microcontroller ground and reference voltage levels since equal noise on these do not affect the differential signal
- Double dynamic range compared to single-ended operation since the allowed input range is symmetric around 0V instead of being limited to positive values only
- Provides good performance even for small voltage signals due to strong noise rejection
- Can be used to measure single-ended signals by connecting the sensor ground level to the negative input of the differential pair
- Compared to using operational amplifiers to transform a differential signal for single-ended conversion, a differential ADC offers end-to-end differential signaling through an integrated and more robust solution
- If a sensor provides a small single-ended signal with a large DC-offset, a differential ADC could utilize more of the available resolution by connecting a corresponding DC-voltage to one of the differential inputs and setting the voltage reference to match the signal, while a single-ended ADC would need to use a voltage reference large enough to include both the DC-offset and the actual signal

Main drawbacks:

- · Sensors and microcontrollers are commonly not available in the lowest price ranges
- · Requires two microcontroller input pins per sensor compared to one for single-ended operation
- · Somewhat more complex to connect and use
- · Compared to single-ended sensors, fewer sensors provide a native differential output

### 2.3 Typical Applications

Below are some specific microcontroller applications where differential signaling and conversion are commonly used:

- Thermocouple-based temperature measurement
- Strain gauge-based force sensing
- Resistor bridge-based pressure sensing
- Applications in environments with electromagnetic and radio frequency noise
- · Applications that require long signal paths between sensors and microcontroller
- Current measurements

### 3. Considerations

There will always be some level of noise on the analog signal for any kind of A/D conversion. Consider the possible noise magnitude when evaluating the maximum dynamic range of the input signal. The output will saturate, and information will be lost if the input, including noise, exceeds the ADC voltage reference. It might be harmful to the microcontroller if it exceeds the allowed pin voltage range.

To improve resolution utilization when using an ADC with a configurable voltage reference, evaluate the maximum dynamic range of the input signal including noise and select a reference level that encompasses it as tightly as possible without limiting it.

For both single-ended and differential conversion, the magnitude of the final result is the ratio between input magnitude and reference voltage level. Consequently, not only noise on the signal itself but also noise on the microcontroller ground level and ADC voltage reference will affect the converted value.

A shorter analog signal path will most likely pick up less noise. This is especially important for single-ended signals.

A microcontroller with a differential ADC does not necessarily allow a total input range of  $-V_{CC}$  to  $V_{CC}$ . Make sure the selected voltage reference is within the allowed pin voltage range. If the ADC supports both single-ended and differential operation, a voltage reference close to  $V_{CC}$  could be inside the allowed range in single-ended mode, but outside specifications in differential mode.

If a differential sensor and the microcontroller are electrically isolated, the signal could be allowed to have a DC voltage outside the rated range for the microcontroller.

# 4. Revision History

Doc. Rev.	Date	Comments
A	08/2019	Initial document release

### The Microchip Website

Microchip provides online support via our website at http://www.microchip.com/. This website is used to make files and information easily available to customers. Some of the content available includes:

- **Product Support** Data sheets and errata, application notes and sample programs, design resources, user's guides and hardware support documents, latest software releases and archived software
- General Technical Support Frequently Asked Questions (FAQs), technical support requests, online discussion groups, Microchip design partner program member listing
- **Business of Microchip** Product selector and ordering guides, latest Microchip press releases, listing of seminars and events, listings of Microchip sales offices, distributors and factory representatives

## **Product Change Notification Service**

Microchip's product change notification service helps keep customers current on Microchip products. Subscribers will receive email notification whenever there are changes, updates, revisions or errata related to a specified product family or development tool of interest.

To register, go to http://www.microchip.com/pcn and follow the registration instructions.

# **Customer Support**

Users of Microchip products can receive assistance through several channels:

- Distributor or Representative
- Local Sales Office
- Embedded Solutions Engineer (ESE)
- Technical Support

Customers should contact their distributor, representative or ESE for support. Local sales offices are also available to help customers. A listing of sales offices and locations is included in this document.

Technical support is available through the website at: http://www.microchip.com/support

### **Product Identification System**

To order or obtain information, e.g., on pricing or delivery, refer to the factory or the listed sales office.

## **Microchip Devices Code Protection Feature**

Note the following details of the code protection feature on Microchip devices:

- · Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

### Legal Notice

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights unless otherwise stated.

### Trademarks

The Microchip name and logo, the Microchip logo, Adaptec, AnyRate, AVR, AVR logo, AVR Freaks, BesTime, BitCloud, chipKIT, chipKIT logo, CryptoMemory, CryptoRF, dsPIC, FlashFlex, flexPWR, HELDO, IGLOO, JukeBlox, KeeLoq, Kleer, LANCheck, LinkMD, maXStylus, maXTouch, MediaLB, megaAVR, Microsemi, Microsemi logo, MOST, MOST logo, MPLAB, OptoLyzer, PackeTime, PIC, picoPower, PICSTART, PIC32 logo, PolarFire, Prochip Designer, QTouch, SAM-BA, SenGenuity, SpyNIC, SST, SST Logo, SuperFlash, Symmetricom, SyncServer, Tachyon, TempTrackr, TimeSource, tinyAVR, UNI/O, Vectron, and XMEGA are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

APT, ClockWorks, The Embedded Control Solutions Company, EtherSynch, FlashTec, Hyper Speed Control, HyperLight Load, IntelliMOS, Libero, motorBench, mTouch, Powermite 3, Precision Edge, ProASIC, ProASIC Plus, ProASIC Plus logo, Quiet-Wire, SmartFusion, SyncWorld, Temux, TimeCesium, TimeHub, TimePictra, TimeProvider, Vite, WinPath, and ZL are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Adjacent Key Suppression, AKS, Analog-for-the-Digital Age, Any Capacitor, AnyIn, AnyOut, BlueSky, BodyCom, CodeGuard, CryptoAuthentication, CryptoAutomotive, CryptoCompanion, CryptoController, dsPICDEM, dsPICDEM.net, Dynamic Average Matching, DAM, ECAN, EtherGREEN, In-Circuit Serial Programming, ICSP, INICnet, Inter-Chip Connectivity, JitterBlocker, KleerNet, KleerNet Iogo, memBrain, Mindi, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICkit, PICtail, PowerSmart, PureSilicon, QMatrix, REAL ICE, Ripple Blocker, SAM-ICE, Serial Quad I/O, SMART-I.S., SQI, SuperSwitcher, SuperSwitcher II, Total Endurance, TSHARC, USBCheck, VariSense, ViewSpan, WiperLock, Wireless DNA, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

The Adaptec logo, Frequency on Demand, Silicon Storage Technology, and Symmcom are registered trademarks of Microchip Technology Inc. in other countries.

GestIC is a registered trademark of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

<sup>©</sup> 2019, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

ISBN: 978-1-5224-4887-7

AMBA, Arm, Arm7, Arm7TDMI, Arm9, Arm11, Artisan, big.LITTLE, Cordio, CoreLink, CoreSight, Cortex, DesignStart, DynamIQ, Jazelle, Keil, Mali, Mbed, Mbed Enabled, NEON, POP, RealView, SecurCore, Socrates, Thumb, TrustZone, ULINK, ULINK2, ULINK-ME, ULINK-PLUS, ULINKpro, μVision, Versatile are trademarks or registered trademarks of Arm Limited (or its subsidiaries) in the US and/or elsewhere.

### **Quality Management System**

For information regarding Microchip's Quality Management Systems, please visit http://www.microchip.com/quality.



# **Worldwide Sales and Service**

AMERICAS	ASIA/PACIFIC	ASIA/PACIFIC	EUROPE
Corporate Office	Australia - Sydnev	India - Bangalore	Austria - Wels
2355 West Chandler Blvd.	Tel: 61-2-9868-6733	Tel: 91-80-3090-4444	Tel: 43-7242-2244-39
Chandler, AZ 85224-6199	China - Beiiing	India - New Delhi	Fax: 43-7242-2244-393
Tel: 480-792-7200	Tel: 86-10-8569-7000	Tel: 91-11-4160-8631	Denmark - Copenhagen
Fax: 480-792-7277	China - Chengdu	India - Pune	Tel: 45-4450-2828
Technical Support:	Tel: 86-28-8665-5511	Tel: 91-20-4121-0141	Fax: 45-4485-2829
http://www.microchip.com/support	China - Chongging	Japan - Osaka	Finland - Espoo
Web Address:	Tel: 86-23-8980-9588	Tel: 81-6-6152-7160	Tel: 358-9-4520-820
http://www.microchip.com	China - Dongguan	Japan - Tokyo	France - Paris
Atlanta	Tel: 86-769-8702-9880	Tel: 81-3-6880- 3770	Tel: 33-1-69-53-63-20
Duluth. GA	China - Guangzhou	Korea - Daegu	Fax: 33-1-69-30-90-79
Tel: 678-957-9614	Tel: 86-20-8755-8029	Tel: 82-53-744-4301	Germany - Garching
Fax: 678-957-1455	China - Hangzhou	Korea - Seoul	Tel: 49-8931-9700
Austin. TX	Tel: 86-571-8792-8115	Tel: 82-2-554-7200	Germany - Haan
Tel: 512-257-3370	China - Hong Kong SAR	Malaysia - Kuala Lumpur	Tel: 49-2129-3766400
Boston	Tel: 852-2943-5100	Tel: 60-3-7651-7906	Germany - Heilbronn
Westborough MA	China - Naniing	Malaysia - Penang	Tel: 49-7131-72400
Tel: 774-760-0087	Tel: 86-25-8473-2460	Tel: 60-4-227-8870	Germany - Karlsruhe
Eax: 774-760-0088	China - Qingdao	Philippines - Manila	Tel: 49-721-625370
Chicago	Tel: 86-532-8502-7355	Tel: 63-2-634-9065	Germany - Munich
Itasca II	China - Shanghai	Singapore	Tel: 49-89-627-144-0
Tel: 630-285-0071	Tel: 86-21-3326-8000	Tel: 65-6334-8870	Fax: 10-80-627-144-0
Eax: 630-285-0075	China - Shenyang	Taiwan - Hein Chu	Germany - Rosenheim
Dallas	Tel: 86-24-2334-2820	Tel: 886-3-577-8366	Tel: 49-8031-354-560
Addison TX	China - Shenzhen	Taiwan - Kaobsiung	Israel - Rajanana
Tel: 072-818-7/23	Tel: 86-755-8864-2200	Tel: 886-7-213-7830	Tel: 072-0-744-7705
Eax: 072 818 2024	China Suzhou		Italy Milan
Detroit	Tal: 86 186 6233 1526		Tal: 30 0331 742611
Novi MI	China - Wuhan	Thailand - Bangkok	Fax: 30-0331-/66781
Tol: 248 848 4000	Tol: 86 27 5080 5300	Tal: 66.2.604.1351	Italy Badova
	China Vian	Vietnam Ho Chi Minh	Tal: 30 040 7625286
Tol: 281 804 5083		Tol: 84 28 5448 2100	Nothorlands Drupon
Indiananolis	China - Xiamen	Tel. 04-20-3440-2100	Tel: 31-416-600300
Noblesville IN	Tel: 86-502-2388138		Fax: 31-416-690340
Tal: 217 772 8222	China Zhuhai		Norway Trandhaim
Fox: 217 772 5452			
Tal: 317 526 2380	161. 00-7 30-32 10040		Boland Warsaw
			Tol: 48 22 3325737
			Bomania Bucharost
Tal: 0/0_/62_0523			Tel: 10-21-107-87.50
Tel: 949-402-9525			Tel. 40-21-407-87-50
Fax. 949-402-9000			Tal: 24 01 708 08 00
Balaigh NC			Fey: 24 01 708 09 01
Tal: 010 844 7510			Fax. 34-91-708-08-91
101. 919-044-7010			Tal: 46 31 704 60 40
Tal: 631 435 6000			Sweden Stockholm
101.031-433-0000			
Jan JUSE, CA			161. 40-0-2090-4024
Tel: 408-735-9110			
Canada - Toronto			Fax: 44-118-921-5820
Iei: 905-695-1980			
Fax. 905-095-2078			